Private Circuits

Yury Lifshits

Steklov Institute of Mathematics, St.Petersburg, Russia yura@logic.pdmi.ras.ru

Tartu University 16/03/2006

Yury Lifshits (Steklov Inst. of Math) Private Circuits Tartu'06 1 / 20

Outline

- 1 Private circuits: Definition and Motivation
- 2 Secret Sharing Construction
- 3 Fake Chanels Construction

Yury Lifshits (Steklov Inst. of Math) Private Circuits Tartu'06 3 / 20

Security Against Probing Attacks

Adversary is able to listen up to t wires

Perfect security: distribution of any t wires is independed on input

Statistical security: for any fixed t-attack it is a negligible chance over a random execution that observable distribution differs with secure (independed from input) distribution

Yury Lifshits (Steklov Inst. of Math)

Private Circuits

Tartu'06 5 / 20

Motivation

Main application:

Protection hardware realizations of block cyphers (AES,...) with embedded key from probing attacks

Outline

- Private circuits: Definition and Motivation
- Secret Sharing Construction
- Sake Chanels Construction

ury Lifshits (Steklov Inst. of Math) Private Circuits Tartu'06 2 / 20

Boolean circuits

Who are boolean circuits?

- Input wires
- AND and NOT gates
- Random bit gates
- Sometimes, memory

rry Lifshits (Steklov Inst. of Math) Private Circuits Tartu'06 4 / 20

Proposed Solution

Transform any circuit C to I, C', D

- I: very simple encoding block. Adversary not allowed to listen internal wires
- *O*: very simple decoding block. Adversary not allowed to listen internal wires
- ullet C': transformation image of C. Adwersary can listen up to t wires on execution

Yury Lifshits (Steklov Inst. of Math) Private Circuits Tartu'06 6 / 20

Outline

- 1 Private circuits: Definition and Motivation
- 2 Secret Sharing Construction
- Fake Chanels Construction

rry Lifshits (Steklov Inst. of Math)
Private Circuits
Tartu'06 7 / 20
Yury Lifshits (Steklov Inst. of Math)
Private Circuits
Tartu'06 8 / 20

Basic Idea

Any ideas?

Trivial (still working) approach: use t+1 wires in C' for each wire in C. For simplicity of further proof we use m = 2t + 1 wires

Are we done? What do we need?

How to compute gates? What Encoding/Decoding to use?

AND Gate

We need to compute encoding for $c = \sum_{i,j} a_i b_j$

We take the following encoding:

$$c_i = a_i b_i \oplus_{j \neq i} z_{i,j},$$

where for i < j we take $z_{i,j}$ at random, while for i > j we take

$$z_{i,j} = (z_{j,i} \oplus a_i b_j) \oplus a_j b_i$$

Tartu'06 11 / 20

Outline

- Private circuits: Definition and Motivation
- Secret Sharing Construction
- Fake Chanels Construction

Tartu'06 13 / 20

Refreshing Effect

Observation over secret sharing construction: t/2 observations even for every gate provide no information on original data

Proof: refreshing effect

NOT Gate

Encoding:

Encode input bit b_i to $r_1, \ldots, r_{2t}, b_i \oplus_{j=1}^{2t} r_j$

Decoding:

Decode output bit $c_i = \bigoplus_{j=1}^{2t+1} w_j$

NOT gate:

Apply not to first wire in a bundle

Security/Cost Analysis

Claim: Fixing up to t values of $a_i, b_j, a_i b_j, z_{i,j}, c_j$ provides no

information on a, b and c

Cost: $|C'| = t^2 |C|$

Tartu'06 12 / 20

Statistical Security

Two parameters: security parameter k and adversary power t

Statistical security:

For any fixed t-attack

chance over a random execution that

observable distribution differs with independed from input distribution is negligible (in terms of k)

Our goal: $t \cdot poly(k)$ cost

Tartu'06 14 / 20

Step 1: Security Against Random Attack

Random attack: adversary is able to observe each wire with probability 1/10k

Take secret sharing construction for k adversary power

- To broke a circuit advesary need $k/2 >> \frac{1}{10k}k^2$ wires in some
- Probability calculations shows that this has a negligible chance

Tartu'06 15 / 20 Tartu'06 16 / 20

Step 2: Security Against Worst Case Attack

Final step: to force any attack no more effective than random attack

- Split every wire to s wires
- ullet Only one contain 0/1 information
- ◆ All others contain special symbol ★
- A meaningful channel is elected in run time

Home Problem 5

HP5: Invent a n^2 sorting circuit (one gate sorts two elements)

Comment on Home Problem 4: prove that probability is smaller than 1/m from some m_0

Deadline 1: tomorrow lecture, 17/03/2006 — 16-15

Deadline 2: 31/03/2006 — 16-15

Summary

Main points:

- ullet New model of hardware attack: up to t wires are observed by adversary
- Two types of data security: perfect nad statistical
- ullet Cost of protecting transformation is $t^2|C|$ and $t\operatorname{poly}(k)|C|$ correspondingly

Reading List

Y. Ishai, A. Sahai, D. Wagner
Private circuits: securing hardware against probing attacks, 2003.
http://www.cs.ucla.edu/~sahai/work/privcirc-crypto03.ps

Thanks for attention. Questions?